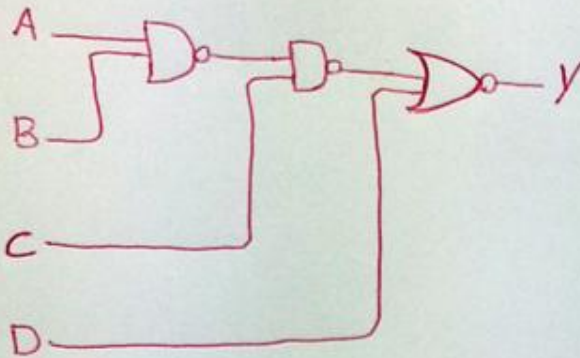


1. Draw the circuit diagram for the Boolean expression:

$$Y = (((A.B)'.C)' + D)'$$



2. Obtain the truth table of the following Boolean expression:

$$Y = A'BC + A'B'C' + B'C + C' + ABC$$

Method

$$Y = BC(A + A') + C'(A'B' + 1) + B'C$$

$$= BC + C' + B'C$$

$$= C(B + B') + C'$$

$$= C + C'$$

$$= \boxed{1}$$

A	B	C	Y	Case num.
0	0	0	1	①
0	0	1	1	②
0	1	0	1	③
0	1	1	1	④
1	0	0	1	⑤
1	0	1	1	⑥
1	1	0	1	⑦
1	1	1	1	⑧

$$Y = A'BC + A'B'C' + B'C + C' + ABC$$

Cases where
 $Y=1$

④

①

②

⑥

①

③

⑤

⑦

⑧